



# IDE ASSIGNMENT

TANGALLAMUDI RAMA SAI  
 ramsaitangallamudi19@gmail.com  
 IITH - Future Wireless Communications (FWC)

## CONTENTS

1	Question	2
2	Components	2
3	Connections	2
4	Procedure	2
5	Output	2

### 1 Question

- 1) A 2-bit synchronous counter using two J-K flip flops is shown. The expressions for the inputs to the J-K flip flops are also shown in the figure. The output sequence of the counter starting from  $Q_1Q_2 = 00$  is

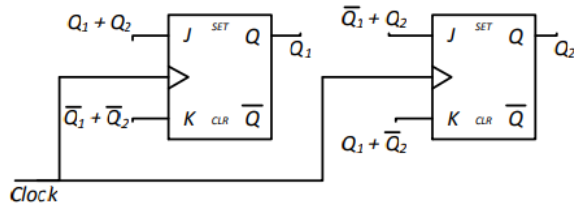


Fig. 1: 2-bit synchronous counter

- a)  $00 \rightarrow 11 \rightarrow 10 \rightarrow 01 \rightarrow 00 \dots$   
 b)  $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \dots$   
 c)  $00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00 \dots$   
 d)  $00 \rightarrow 10 \rightarrow 11 \rightarrow 01 \rightarrow 00 \dots$

### 2 Components

Component	Values	Quantity
Arduino	UNO	1
JumperWires	M-F	25
JK-Flip flop	7476	1
OR Gate	7432	1
Bread board		1

### 3 Connections

Arduino	7476(JK Flipflop)	7432(OR Gate)
D13	CLK1	
	PRESET	
	CLEAR	
	J1	3
5V	VCC	VCC
D13	CLK2	
	PRESET	
	CLEAR	
	J2	6
	!Q2	5,9
	Q2	2,12
	K2	8
GND	GND	GND
	!Q1	4,13
	Q1	1,10
	K1	11

Fig. 2: Connections

### 4 Procedure

- 1) Connect the circuit as per the above table.  
 2) Connect the LED's to see the binary output sequence 0, 1, 3, 2

<https://github.com/Tangallamudi-RamaSai/Platformio/blob/main/platformio.ino.ino>

### 5 Output

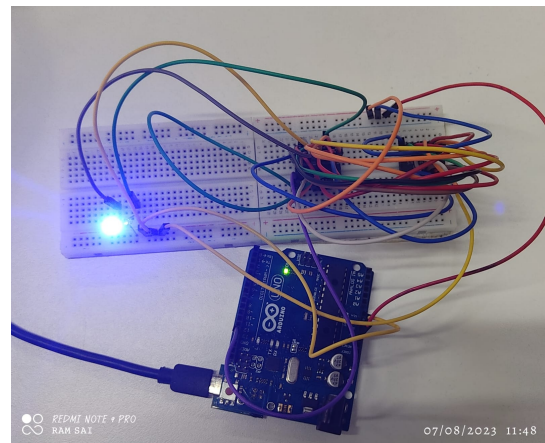


Fig. 3: Output